

Student Name: \_\_\_\_\_

Reg. No. \_\_\_\_\_

2019-EE-383

## EE110 Circuit Analysis and Design

Fall 2022, Session 2021 (3<sup>rd</sup> Semester)

Final Exams


Time Allowed: 90 Minutes

Total Marks: 40

- All the related parts of a question must be solved together.
- Understanding of question is part of exam.


Q.1 Analyze the circuit in figure below and use Laplace/Inverse Laplace to find  $v_C(t)$ .

10

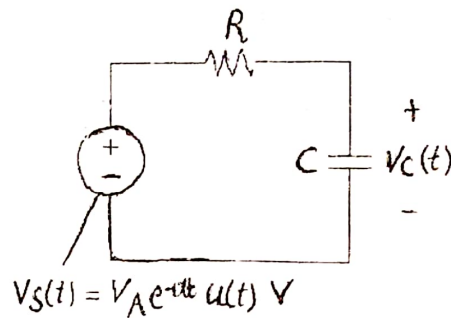

CLO2

Q.2 Evaluate the circuit in figure below and:

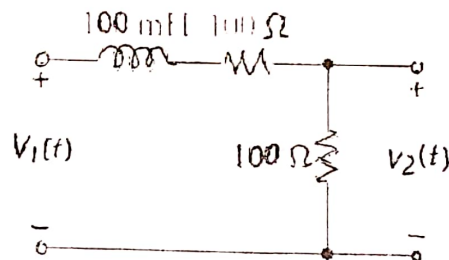

CLO3

A Find the transfer function  $T_V(s) = V_2(s)/V_1(s)$

1

B Find the DC gain, infinity frequency gain, and cut-off frequency. Identify the type of gain response.

4


C Sketch the straight line approximations of the gain and phase responses (Bode plots).

4

D Calculate the gain at  $\omega = 0.5\omega_c$  and  $2\omega_c$

1


Q.3 The switch in circuit of figure below has been closed for a long time. At  $t = 0$  the switch is suddenly opened.

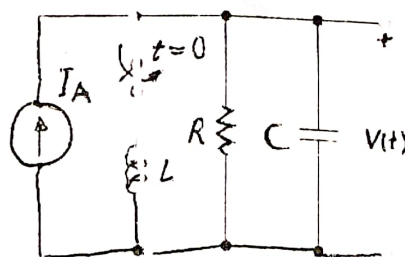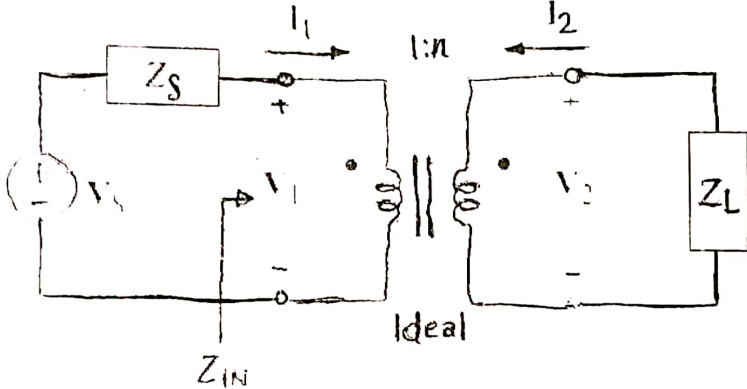

CLO3

Student Name: \_\_\_\_\_

Reg. No. \_\_\_\_\_

	A Evaluate the circuit to find the transform $I_R(s)$ for the current through the resistor (Use Circuit Transformation).	7
	B Select values of R, L and C so that the current reaches at least 63% of its final value in 100ms or less.	3
Q.4	<p>The turns ratio of the ideal transformer in figure below is <math>n = 5</math>. The source and load impedances are <math>Z_S = 2.5 + j1.5 \Omega</math> and <math>Z_L = 75 + j10 \Omega</math>. Analyze the circuit to find <math>I_1</math>, <math>V_1</math>, <math>I_2</math> and <math>V_2</math> when the input is <math>V_S = 220 \angle 0^\circ \text{ V}</math>.</p> 	10

CLO4