

Student Name: _____

Reg. No. 2019EE-383


EE110 Circuit Analysis and Design

Fall 2022, Session 2021 (3rd Semester)

Mid Exam

- > All the related parts of a question must be solved together.
- > Understanding of question is part of exam.

Time Allowed: 60 Minutes
Total Marks: 30

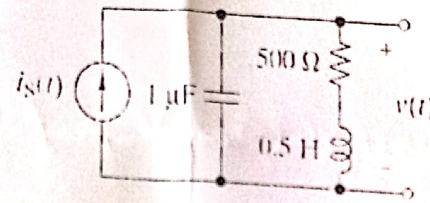Q.1	In a series RLC circuit the zero-input voltage across the $1\text{-}\mu\text{F}$ capacitor is $v_c(t) = 10e^{-1000t} \sin 2000t \text{ V} \quad t \geq 0$		
	A Analyze the response and find the circuit characteristic equation	3	CLO1
	B Find R and L	4	
	C Find $i_L(t)$ for $t \geq 0$	2	
	D Find the initial values of the state variables	1	
Q.2	The circuit in Figure below is operating in the sinusoidal steady state with $i_s(t) = 100 \cos(1000t - 45^\circ) \text{ mA}$		
			
	A Analyze the circuit and transform it into phasor domain	2	CLO2
	B Solve for the phasor voltage V	3	
	C Solve for the phasor current through each element	3	
	D Find the waveforms corresponding to the phasors found in (b) and (c)	2	
Q.3	A The two sources in Figure below have the same frequency. Analyze the circuit and use superposition to find the phasor current I_x	10	
	